

**BONAM VENKATA CHALAMAYYA INSTITUTE OF TECHNOLOGY &
SCIENCE**

(AUTONOMOUS)

I - B. Tech II-Semester Supplementary Examinations (BR23), Sep/Oct - 2024
BASIC ELECTRICAL AND ELECTRONICS ENGINEERING (CSE.CSE-AI&DS, AI&ML)

Time: 3 hours

Max. Marks: 70

Question Paper consists of Part-A and Part-B
Answer ALL the question in Part-A and Part-B

PART-A (1 X 5 = 5M)

	Marks	CO	BL
1. a) State the limitations of superposition theorem?	(1M)	1	1
b) A single ac waveform has an rms value of 230 V and 50 HZ frequency? Draw the waveform indicating peak value and time period?	(1M)	2	2
c) Write few applications of AC machines	(1M)	2	2
d) What is voltage and frequency of 1-phase supply in India?	(1M)	3	1
e) Write the function of fuse	(1M)	3	2
<u>(10 X 3 = 30M)</u>			
2.a) Write down the expression for active and apparent power?	10(M)	1	3
(OR)			
b) Derive the expression RMS value of sinusoidal wave form $v(t) = V_m \sin \omega t$.	10(M)	3	3
3.a) Explain the working principle of three phase induction generator?	10(M)	2	3
(OR)			
b) Illustrate the principle of working of a PMMC instrument with neat diagram.	10(M)	2	3
4.a) Explain the operation of solar power generation	10(M)	3	3
(OR)			
b) Sketch and explain Pipe Earthing	10(M)	4	3

PART-B (1 X 5 = 5M)

	Marks	CO	BL
1. a) What is the application of Zener diode?	(1M)	1	1
b) Name the different configurations of transistor?	(1M)	1	1
c) Draw the block diagram of electronic commutation?	(1M)	2	1
d) Name the universal gates?	(1M)	3	1
e) Write the difference between sequential and combinational circuit?	(1M)	3	1

(10 X 3 = 30M)

- 2.a) Compare PN junction diode and Zener diode and list the applications of Zener diode. 10(M) 1 3
- (OR)
- b) Draw and explain the input and output characteristics of a transistor in CE configuration 10(M) 1 3
- 3.a) Illustrate the operation of full wave rectifier with neat sketch. 10(M) 2 3
- (OR)
- b) Draw the block diagram of an electronic instrumentation system and explain its working 10(M) 2 3
- 4.a) Convert the following number system into indicated system. i) $(256)_{10} = (\dots\dots\dots)_2$ 10(M) 3 3
ii) $(F32C)_{16} = (\dots\dots\dots)_{10}$
- (OR)
- b) Explain the principle of JK flip flop with the help of a block diagram and truth table 10(M) 3 3
