

*Question Paper consists of Part-A and Part-B  
Answer ALL the question in **Part-A and Part-B***

**PART-A (10X2 = 20M)**

		Marks	CO	BL
1. a)	Convert the following.i. $(AB.CD)_{16} = ( )_{10}$ ii. $(123.321)_8 = ( )_{10}$	(2M)	CO1	BL3
b)	Perform the following subtraction in binary using 1's and 2's complement method: $(677)_{10} - (899)_{10}$	(2M)	CO1	BL3
c)	Implement the following function using only NOR gates $F=a.(b+c.d) + (b.c)$	(2M)	CO2	BL3
d)	Design Half Adder and Draw the logic Diagram with its Truth Table	(2M)	CO2	BL2
e)	Design and implement a two bit comparator using logic gates	(2M)	CO3	BL2
f)	Design a 1:8 demultiplexer using two 1:4 demultiplexer.	(2M)	CO3	BL2
g)	What are the differences between Latches and Flip Flops	(2M)	CO4	BL2
h)	Write the differences between combinational and sequential circuits.	(2M)	CO4	BL2
i)	Draw the logic diagram of Meelay and Moore models and also explain their operation with examples	(2M)	CO5	BL2
j)	Explain the procedure of Meelay to Moore conversion.	(2M)	CO5	BL2

**PART-B (5X10 = 50M)**

2a.	Given the 8 bit data word 01011011, generate the 12 bit composite word for the hamming code that corrects and detects single errors.	5(M)	CO1	BL3
b.	Convert the Boolean function $F(A,B,C,D) = A+BC+ACD$ into standard POS form.	5(M)	CO1	BL3
(OR)				
3a.	Perform the following addition using excess-3 code i)386+756 ii)254+ 579	5(M)	CO1	BL3
b.	A 7 bit Hamming code is received as 1110101.Is there any error? If yes, locate the position of the error bit. Parity checks are created by odd parity.	5(M)	CO1	BL3

4a.	Using the Quine–McCluskey tabular method, find the minimum sum of products for $F(A,B,C,D,E) = \sum m(1,5,6,7,9,13,14,15,17,18,19,21,22,23,25,29,30)$	5(M)	CO2	BL3
b.	Design a BCD adder circuit and explain its operation	5(M)	CO2	BL3
(OR)				

5a.	Design a circuit to convert BCD code to Excess 3 code using discrete Logic gates.	5(M)	CO2	BL2
b.	Simplify the following using K- map and implement the same using NAND gates. $Y(A, B, C, D, E) = \sum m(0, 2, 4, 5, 6, 7, 11, 14, 16, 20, 24, 26, 29, 31) + d(9, 12, 18, 27)$	5(M)	CO2	BL2

6a.	Tabulate the PLA programming table for the four Boolean functions listed below $A(x, y, z) = \sum m(1, 2, 4, 6)$ $B(x, y, z) = \sum m(0, 1, 6, 7)$ $C(x, y, z) = \sum m(2, 6)$ $D(x, y, z) = \sum m(1, 2, 3, 5, 7)$	5(M)	CO3	BL3
b.	Realize the function $f(A, B, C, D) = \sum(1, 3, 4, 6, 7, 8, 10, 13, 15)$ using i) 16:1 MUX ii) 8:1 MUX	5(M)	CO3	BL3
(OR)				
7a.	Implement the following functions using a PROM i) $F(w, x, y, z) = \sum(1, 9, 12, 15)$ ii) $G(w, x, y, z) = \sum(0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 12, 13, 14, 15)$	5(M)	CO3	BL3
b.	Define decoder. Construct IC74LS138 decoder using logic gates and truth table	5(M)	CO3	BL2

8a.	Draw the logic diagram of a SR latch using NOR gates. Explain its Operation using excitation table	5(M)	CO4	BL2
b.	Convert D flip-flop into T and JK flip-flops.	5(M)	CO4	BL2
(OR)				
9a.	Draw and explain the logic diagram for a 4-bit binary ripple down counter using positive edge triggered flip-flops	5(M)	CO4	BL2
b.	Draw a 4-bit bi-directional shift register logic diagram and explain its operation	5(M)	CO4	BL2

10a	Reduce the number of states in the following state table and tabulate the reduced state table.	10(M)	CO5	BL3																													
<table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th rowspan="2">PS</th> <th colspan="2">NS, O/P</th> </tr> <tr> <th>X=0</th> <th>X=1</th> </tr> </thead> <tbody> <tr> <td>a</td> <td>f, 0</td> <td>b, 0</td> </tr> <tr> <td>b</td> <td>d, 0</td> <td>c, 0</td> </tr> <tr> <td>c</td> <td>f, 0</td> <td>e, 0</td> </tr> <tr> <td>d</td> <td>g, 1</td> <td>a, 0</td> </tr> <tr> <td>e</td> <td>d, 0</td> <td>c, 0</td> </tr> <tr> <td>f</td> <td>f, 1</td> <td>b, 1</td> </tr> <tr> <td>g</td> <td>g, 0</td> <td>h, 1</td> </tr> <tr> <td>h</td> <td>g, 1</td> <td>a, 0</td> </tr> </tbody> </table>					PS	NS, O/P		X=0	X=1	a	f, 0	b, 0	b	d, 0	c, 0	c	f, 0	e, 0	d	g, 1	a, 0	e	d, 0	c, 0	f	f, 1	b, 1	g	g, 0	h, 1	h	g, 1	a, 0
PS	NS, O/P																																
	X=0				X=1																												
a	f, 0				b, 0																												
b	d, 0				c, 0																												
c	f, 0				e, 0																												
d	g, 1				a, 0																												
e	d, 0				c, 0																												
f	f, 1				b, 1																												
g	g, 0	h, 1																															
h	g, 1	a, 0																															
(OR)																																	
11a	Convert the following Mealy machine into a corresponding Moore machine:																																

PS	NS,Z	
	X=0	X=1
A	C,0	B,0
B	A,1	D,0
C	B,1	A,1
D	D,1	C,0

5(M)

CO5


BL3

b. A sequential circuit has one input and one output .The state diagram is shown below. Design the sequential circuit with D flip-flops

5(M)

CO5

BL3

 

\*\*\*\*\*