

Course Code: 23EC5E01

BONAM VENKATA CHALAMAYYA INSTITUTE OF TECHNOLOGY & SCIENCE
(AUTONOMOUS)

III - B.Tech I-Semester Regular Examinations (BR23), Nov/Dec - 2025

ELECTRONIC DEVICES AND CIRCUITS (CSE AI&DS, AI&ML)

Time: 3 hours

Max. Marks: 70

Question Paper consists of Part-A and Part-B
Answer ALL the question in Part-A and Part-B

PART-A (10X2 = 20M)

		Marks	CO	BL
1. a)	Write continuity equation?	(2M)	CO1	BL1
b)	What is zener break down ?	(2M)	CO1	BL1
c)	What is an LED? Write applications of LED?	(2M)	CO2	BL1
d)	What are the advantages of bridge rectifier over full wave rectifier?	(2M)	CO2	BL1
e)	Why n channel MOSFET Preferred over p channel MOSFET?	(2M)	CO3	BL1
f)	What is early effect?	(2M)	CO3	BL1
g)	What is the need of transistor biasing?	(2M)	CO4	BL1
h)	What is thermal runaway and thermal stability?	(2M)	CO4	BL1
i)	Write the advantages h parameters?	(2M)	CO5	BL1
j)	Compare CB.CC.CE amplifier configurations?	(2M)	CO5	BL2

PART-B (5X10 = 50M)

2a.	Define hall effect ?Derive an expression for hall coefficient for a semiconductor material.	5(M)	CO1	BL3
b.	Give the mathematical analysis of Fermi level lies in the center of forbidden energy band for an intrinsic semiconductor	5(M)	CO1	BL4
(OR)				
3a.	Derive expression for contact potential in open circuit PN junction Diode?	6(M)	CO1	BL3
b.	Explain the characteristics of PN junction diode in both forward and reverse bias?	5(M)	CO1	BL2
4a.	Explain the operation of tunnel diode with necessary diagrams?	5(M)	CO2	BL2
b.	Discuss principle and operation of silicon controlled rectifier with its characteristics.	5(M)	CO2	BL2
(OR)				
5a.	Derive an expression for ripple factor and efficiency of full wave full wave rectifier.	5(M)	CO2	BL4

b.	Draw the circuit diagram of LC filter and derive its ripple factor.	5(M)	CO2	BL3
----	---------------------------------------------------------------------	------	-----	-----

6a.	Draw and explain the input and output characteristics of BJT In Common emitter configuration	5(M)	CO3	BL3
b.	Explain EBERS MOL MODEL OF Transistor	5(M)	CO3	BL2
(OR)				
7a.	Explain the construction and characteristics FET?	5(M)	CO3	BL3
b.	Comparison between MOSFET and JFET.	5(M)	CO3	BL

8a.	Explain need for biasing in electronic circuits .what are the factors effecting stability factor.	5(M)	CO4	BL2
b.	Why self bias technique is so popular? and derive an expression for stability factor.	5(M)	CO4	BL3
(OR)				
9a.	Explain FET biasing methods	5(M)	CO4	BL2
b.	Draw AC load line and DC load line of a transistor? And determine operating point of transistor.	5(M)	CO4	BL3

10a.	Derive an expression for voltage gain current gain ,input impedance,output admittance with respect source and current gain, with respect generalized transistor amplifier at low frequencies.	10(M)	CO5	BL4
(OR)				
11a.	Using approximate h parameter model of CE obtain the expression for i)AI ii)RI iii)AV iv)RO	6(M)	CO5	BL3
b.	Give the comparison of transistor as amplifiers.	4(M)	CO5	BL2
